

B.Sc. 1st Semester (Honours) Examination-2022-23**ELECTRONICS**

Course ID : 11711 Course Code : SH/ELC/101/C-1T


**Course Title : Basic Circuit Theory and
Network Analysis (New)**

Time : 1 Hour 15 Minutes

Full Marks : 25

*The figures in the right hand margin indicate full marks.**Candidates are required to give their answers in their
own words as far as practicable.*1. Answer **any three** of the following questions : $1 \times 3 = 3$

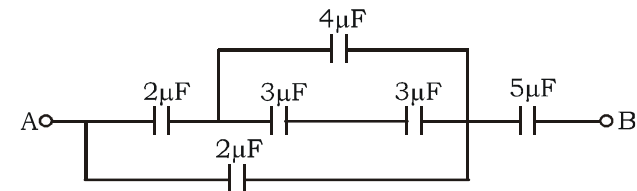- (a) What is equivalent capacitance between terminals A and B of the following network?




- (b) What is the value of the electrical resistance of the resistor with colour rings as follows :
green, blue, yellow and silver.
- (c) A sine wave has a frequency of 50kHz. How many cycles does it complete in 20 msec?
- (d) What do you mean by 'electric circuit' and 'electric network'?
- (e) Mention two limitations of Ohm's law.
- (f) What do you mean by 'linear' and 'non-linear' circuit elements? Give examples.

2. Answer **any three** of the following questions : $2 \times 3 = 6$

- (a) What is the source transformation? Show how a voltage source can be converted into a current source and vice-versa.
- (b) The current and voltage through a certain element is given by $v = 100\sin(314t + 45^\circ)$ and $i = 10 \sin(314t + 315^\circ)$. Identify the circuit element and find its value.

- (c) Define frequency, instantaneous value, effective value and average value for a sinusoidal signal. Find RMS and average value of the given waveform.


2+2+2

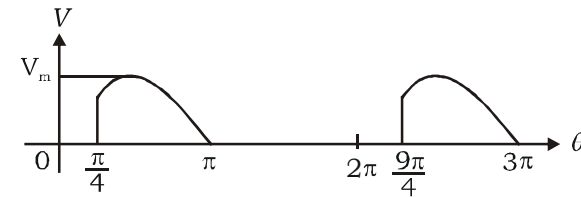

4. Answer **any one** question : $6 \times 1 = 6$


- (a) State Superposition theorem for a dc network. Find the current through 10Ω resistor using this theorem.

2+4

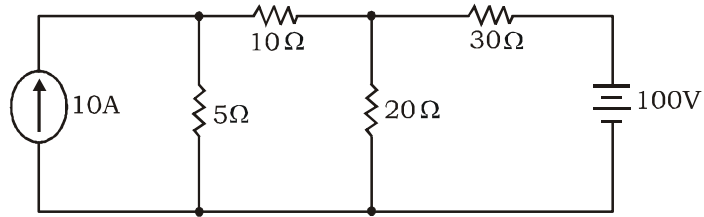

- (b) Find Y parameters for the network shown below. Hence, determine whether the network is symmetrical or reciprocal.

4+2

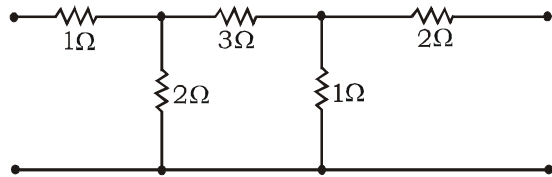

- (c) A series RLC circuit has the following parameters : $R = 10\Omega$, $L = 0.01$ H and $C = 100\mu\text{F}$. Find the lower and upper half-power frequencies of the circuit.

- (d) A voltage of $v(t) = 100 \sin \omega t$ is applied to a circuit. The current flowing through the circuit is $i(t) = 15 \sin(\omega t - 30^\circ)$. Determine the average power delivered by the circuit.


- (e) If $Z_1 = 3 + j7$ and $Z_2 = 12 - j6$ are connected in parallel, then find the equivalent impedance of their combination.

- (f) Explain the following terms : Node, Junction, Branch and Mesh.

3. Answer **any two** of the following questions : $5 \times 2 = 10$


- (a) Derive the relationship to express three delta connected resistances into equivalent star. Hence, find the equivalent resistance between the terminals A and B of the given network.

2+3

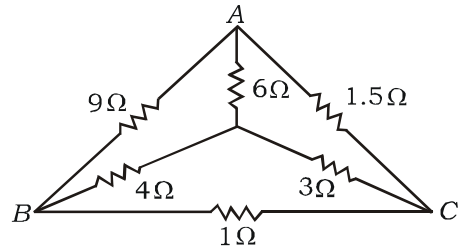


- (b) If the current flowing through R is 3A, find the value of R using i) KVL and ii) KCL.

$$2\frac{1}{2} + 2\frac{1}{2}$$

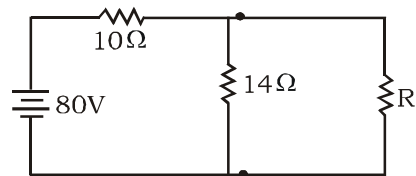

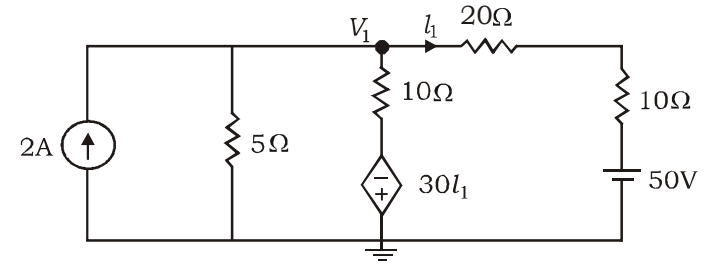- (c) What are dependent sources? Find the voltage across 5Ω resistor in the network shown below. 1+4



- (d) What is a 'supernode'? Using the concept, find the current through 5Ω resistor shown in figure below.

1+4

