

B.Sc. Semester I (Honours) Examination, 2018-19

COMPUTER SCIENCE

Course ID : 11512

Course Code : SHCSC-102C-2(T)

Course Title : Computer System Architecture

Time: 1 Hour 15 Minutes

Full Marks: 25

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

1. Answer *any five* questions from the following: 1×5=5
 - (a) What is demultiplexer?
 - (b) What is sequential circuit?
 - (c) What is RISC?
 - (d) Convert $(E5.D)_{16}$ to binary.
 - (e) What is EPROM?
 - (f) What is 2's complement?
 - (g) What is register?
 - (h) What is counter?

 2. Answer *any two* questions from the following: 5×2=10
 - (a) What is combinational circuit? Distinguish between combinational circuit and sequential circuit. 2+3=5
 - (b) Write down the truth table and logic circuit diagram of J-K flip-flop. 2+3=5
 - (c) Distinguish between RAM and ROM.
 - (d) Write short note on Direct Memory Access (DMA).

 3. Answer *any one* question from the following: 10×1=10
 - (a) What is half-adder? What is full-adder? Design a full-subtractor circuit showing the necessary steps. 2+2+6=10
 - (b) Write short note on different types of system Bus. 10
-