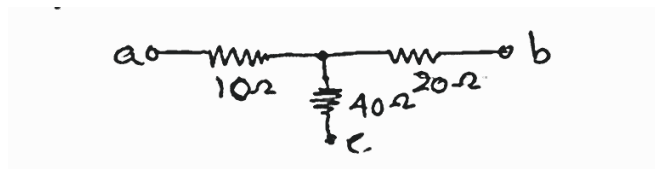



B.Sc. Semester I (Honours) Examination, 2019**ELECTRONICS****Course ID : 11711****Course Code : SHELC-101C-1(T)****Course Title : Basic Circuit Theory and Network Analysis****Time: 1 Hour 15 Minutes****Full Marks: 25***The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*

1. Answer *any three* of the following: 1×3=3
- State one limitation of Ohm's law.
 - Draw V-I characteristics of an ideal voltage source.
 - What is 'node' of a circuit?
 - What is the equivalent capacitance when several capacitances $C_1, C_2, C_3, \dots, C_n$ are connected in series?
 - Draw the symbolic representations of a DC voltage source and a DC current source.
 - A voltage source has internal impedance $(4 + j5)\Omega$. Find the load impedance for maximum power transfer.
2. Answer *any three* of the following: 2×3=6
- What do you mean by dependent and independent sources?
 - What are active and passive circuit elements? Give examples of each.
 - States Kirchoff's Voltage Law (KVL) and Kirchoff's Current Law (KCL).
 - Distinguish between 'mesh' and 'loop' of an electric circuit.
 - In a series RLC circuit, if the value of L and C are $100\mu\text{H}$ and $0.1\mu\text{F}$ respectively, find the resonant frequency in Hz.
 - What is an alternating current? What is period?
3. Answer *any two* of the following: 5×2=10
- Transform the T(star) network to π (Delta) network. 5




- State and prove Thevenin's theorem for dc network. 2+3=5

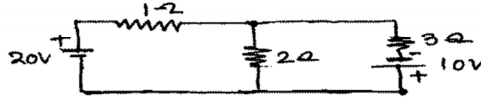- (c) An alternating e.m.f. is applied to a pure inductor and a pure capacitor. Investigate the phase relationship of the alternating current with the alternating e.m.f. in each case. What do you mean by wattless current? 2+2+1=5
- (d) For the circuit shown below, find the currents in each branch by nodal method. 5




4. Answer *any one* of the following: 6×1=6

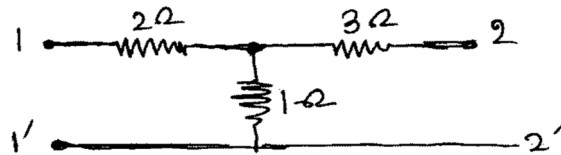- (a) What is two-port network? Find the h-parameters of the two-port network shown below. 2+4=6



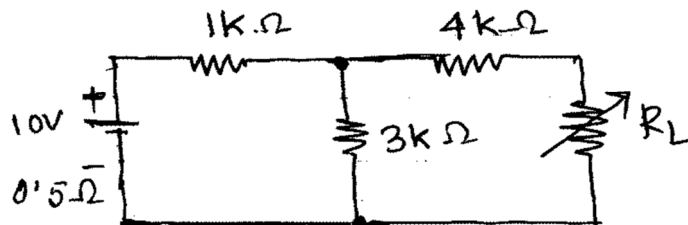- (b) A constant e.m.f. E is applied to a circuit containing a resistor R and a capacitor C in series. Deduce an expression for the charge on the capacitor as a function of time. Define time constant of an RC circuit. 4+2=6
- (c) State Maximum Power Transfer theorem. Find the value of R_L for the circuit shown below so that maximum power is transferred to R_L from battery and hence find the amount of maximum power transferred. 2+2+2=6



B.Sc. Semester I (Honours) Examination, 2019**ELECTRONICS****Course ID : 11712****Course Code : SHELC-102C-2(T)****Course Title : Mathematics Foundation for Electronics****Time: 1 Hour 15 Minutes****Full Marks: 25***The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*

1. Answer *any three* of the following: 1×3=3
- (a) What do you mean by differential equation?
- (b) Give one example of partial differential equation of 2nd order.
- (c) What is 'order' and 'degree' of a differential equation?
- (d) What is a 'singular' point?
- (e) What is recurrence relation?
- (f) Give the definition of Gamma function (Γ).
2. Answer *any three* of the following: 2×3=6
- (a) What is the 'ordinary' point? 2
- (b) What is the origin of 'indicial' equation? 2
- (c) What is the relation between Beta and Gamma functions?
 Show that: $\Gamma(n + 1) = n\Gamma(n) = n!$ 1+1=2
- (d) $\beta(m + 1, n) = \frac{m}{m+n} \cdot \beta(m, n)$ — Prove this from the definition. 2
- (e) What is an analytic function? 2
- (f) Give one example of row matrix and column matrix. 1+1=2
3. Answer *any two* of the following: 5×2=10
- (a) Solve one dimensional heat flow equation:
 $\frac{\partial u}{\partial t} = c^2 \frac{\partial^2 u}{\partial x^2}$ by separation of variables method.
- (b) Show that the polar forms of Cauchy-Riemann (C-R) equation are
 $\frac{\partial u}{\partial r} = \frac{1}{r} \frac{\partial v}{\partial \theta}, \frac{\partial v}{\partial r} = -\frac{\partial u}{\partial \theta}.$

- (c) Construct the recurrence relation by solving given differential equation, by power series method:

$$(1 - x^2) \frac{d^2y}{dx^2} - 2x \frac{dy}{dx} + 2y = 0$$

- (d) Find the eigenvalues and eigenvectors of the matrix $\begin{pmatrix} 5 & 4 \\ 1 & 2 \end{pmatrix}$.

Or,

Obtain the indicial equation for the given Bessel's equation of order 'n'.

$$x^2 \frac{d^2y}{dx^2} + x \frac{dy}{dx} + (x^2 - n^2)y = 0$$

4. Answer *any one* of the following questions: 6×1=6

- (a) Find the value of $\Gamma\left(\frac{1}{2}\right)$ and hence plot the graph of Gamma function for $n = -\infty$ to $+\infty$ (i.e. for whole range.) 3+3=6

- (b) What is Argand's diagram? Draw the Argand diagram for a complex number. State Residue Theorem. What are the various methods of calculation of Residue? (1+2)+(1+2)=6

- (c) Find the diagonal form of matrix

$$A = \begin{pmatrix} -1 & 2 & -2 \\ 1 & 2 & 1 \\ -1 & -1 & 0 \end{pmatrix} \quad 6$$

Or,

Evaluate the given integral using residue theorem

$$I = \int_C \frac{4-3z}{z(z-1)(z-2)} dz$$

where C is a circle with $|z| = 3/2$. 6
