

BANKURA UNIVERSITY

B.Sc. 1th Semester (Honours) Examination, March 2021

Subject: *Electronics (H)*

Course ID: 11714

Course Code: SH/ELC/103/GE-1(TH)

Course Title: *Electronic Circuits and PCB Designing*

Full Marks: 25

Time: 1 Hr 15 Min

(The figures in the right hand side margin indicate marks.

Answer all the questions)

1. Answer *any three* of the following questions 1×3=3
 - a) Define Ohm's law.
 - b) What do you understand by a junction in a semiconductor?
 - c) What is a Rectifier?
 - d) What is load line of a transistor?
 - e) What do you mean by SMT?
 - f) What is a layout?

2. Answer *any three* of the following questions. 2×3=6
 - a) Starting from Ohm's law deduce the conductance and its unit.
 - b) What do you mean by regulated power supply? Explain.
 - c) Explain thermal runaway of a transistor.
 - d) What is a filter? State different kinds of filters. 1+1=2
 - e) What is leakage current of a transistor. Define it. 1+1=2
 - f) Draw the output characteristics of a transistor and explain each domain.

3. Answer *any two* of the following questions. 5×2=10
 - a) State and Explain Kirchoff's Current law. Show that it represents the conservation of charge. 3+2=5
 - b) State and explain maximum power transfer theorem.

- c) State different kinds of transistor biasing. Which one is superior? 4+1=5
- d) Find the expression of ripple factor of a FWR.
4. Answer *any one* of the following questions. 6×1=6
- a) State and explain Thevenin's theorem with example.
- b) Describe the SMT clearly depicting its benefits and limitations.
- c) What is hybrid parameters? Define each. 2+4=6