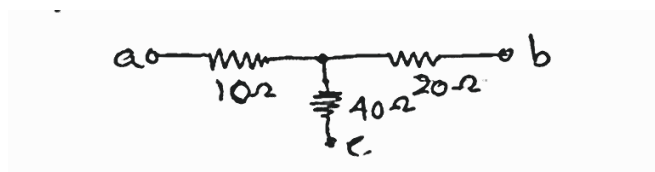



B.Sc. Semester I (Honours) Examination, 2019**ELECTRONICS****Course ID : 11711****Course Code : SHELC-101C-1(T)****Course Title : Basic Circuit Theory and Network Analysis****Time: 1 Hour 15 Minutes****Full Marks: 25***The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*

1. Answer *any three* of the following: 1×3=3
- State one limitation of Ohm's law.
 - Draw V-I characteristics of an ideal voltage source.
 - What is 'node' of a circuit?
 - What is the equivalent capacitance when several capacitances $C_1, C_2, C_3, \dots, C_n$ are connected in series?
 - Draw the symbolic representations of a DC voltage source and a DC current source.
 - A voltage source has internal impedance $(4 + j5)\Omega$. Find the load impedance for maximum power transfer.
2. Answer *any three* of the following: 2×3=6
- What do you mean by dependent and independent sources?
 - What are active and passive circuit elements? Give examples of each.
 - States Kirchoff's Voltage Law (KVL) and Kirchoff's Current Law (KCL).
 - Distinguish between 'mesh' and 'loop' of an electric circuit.
 - In a series RLC circuit, if the value of L and C are $100\mu\text{H}$ and $0.1\mu\text{F}$ respectively, find the resonant frequency in Hz.
 - What is an alternating current? What is period?
3. Answer *any two* of the following: 5×2=10
- Transform the T(star) network to π (Delta) network. 5




- State and prove Thevenin's theorem for dc network. 2+3=5

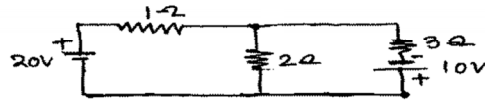- (c) An alternating e.m.f. is applied to a pure inductor and a pure capacitor. Investigate the phase relationship of the alternating current with the alternating e.m.f. in each case. What do you mean by wattless current? 2+2+1=5
- (d) For the circuit shown below, find the currents in each branch by nodal method. 5



4. Answer *any one* of the following: 6×1=6

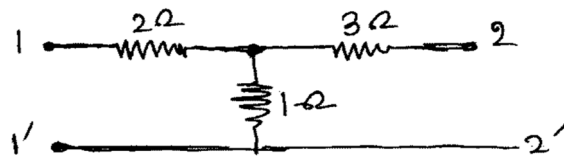- (a) What is two-port network? Find the h-parameters of the two-port network shown below. 2+4=6



- (b) A constant e.m.f. E is applied to a circuit containing a resistor R and a capacitor C in series. Deduce an expression for the charge on the capacitor as a function of time. Define time constant of an RC circuit. 4+2=6
- (c) State Maximum Power Transfer theorem. Find the value of R_L for the circuit shown below so that maximum power is transferred to R_L from battery and hence find the amount of maximum power transferred. 2+2+2=6

