
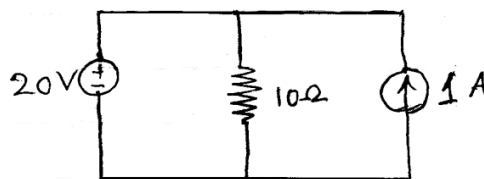


B.Sc. 1st Semester (Honours) Examination, 2019-20**ELECTRONICS****Course ID : 11711****Course Code : SH/ELC/101/C-1****Course Title : Basic Circuit Theory and Network Analysis****Time: 1 Hour 15 Minutes****Full Marks : 25***The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*

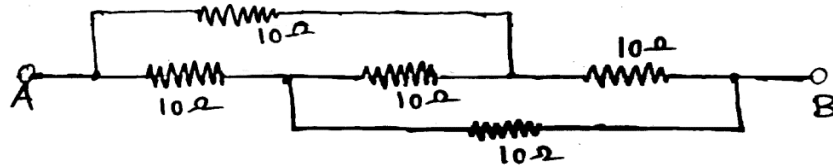
1. Answer *any three* of the following questions: 1×3=3
- What are linear circuit elements?
 - What do you mean by 'Branch' of an electrical network?
 - Define 'cycle' of an alternating voltage.
 - Draw the frequency response curve of an RLC Series Circuit.
 - What are the three types of power used in ac circuit?
 - What is meant by steady state value of a response?
2. Answer *any three* of the following questions: 2×3=6
- What do you mean by ideal current source? Draw its I-V characteristics.
 - Define 'peak value' and 'effective value' of an alternating quantity.
 - Draw the phasor diagram of series R-L circuit.
 - What is an Impedance Triangle?
 - For purely resistive circuit excited by a sinusoidal varying voltage, what are the phase angle and power factor?
 - The resistance of two wires is 25Ω when connected in series and 6Ω when connected in parallel. Calculate the resistance of each wire.
3. Answer *any two* of the following questions: 5×2=10
- State Superposition theorem. Determine the current through 10Ω resistor using this theorem. 2+3=5



- (b) Derive the transient response of series RL circuit with DC input. Sketch the variation of current and voltage across the inductor. 3+1+1=5
- (c) Calculate the resistance between the terminals A-B.



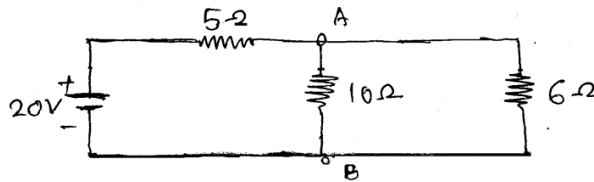- (d) Using Norton's Theorem, find the current through 10Ω resistor for the given network. 5



4. Answer any one of the following questions: 6×1=6

- (a) What are Z-parameters and Y-parameters? Derive the expression for Z-parameters in terms of Y-parameters. 2+4=6
- (b) An RLC Series Circuit consists of $R = 16\Omega$, $L = 0.5\text{mH}$ and $C = 2\mu\text{F}$. Calculate the Quality factor (Q) at resonance, bandwidth and half power frequencies. 2+2+2=6
- (c) Find the current through the branch a-b of the given network using Thevenin's theorem.

