

B.Sc. 3rd Semester (Honours) Examination, 2019-20

ELECTRONICS

Course ID : 31711

Course Code : SH/ELC/301/C-5(T)

Course Title: Electronic Circuits

Time: 1 Hour 15 Minutes

Full Marks: 25

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

1. Answer *any three* of the following questions: 1×3=3
- (a) What is the slope of DC load line in diode circuits?
 - (b) Why h-parameters are called hybrid parameters?
 - (c) What do you mean by 'feed back' in an amplifier circuit?
 - (d) What is rectification?
 - (e) What are clipping circuits?
 - (f) Draw the out-put wave form of a capacitor shunted filter.
2. Answer *any three* of the following questions: 2×3=6
- (a) What is PIV (Peak Inverse Voltage)?
 - (b) What is ac load line? How does it differ from a dc load line in any amplifier circuit?
 - (c) Draw the circuit diagram of Voltage divider method of biasing.
 - (d) What are "Bark hausen criterion for the condition of oscillation"?
 - (e) What are the basic differences between a voltage amplifier and a power amplifier?
 - (f) What is push-pull operation? Where is it used?
3. Answer *any two* of the following questions: 5×2=10
- (a) Derive an expression for voltage gain of a CE amplifier in the midfrequency range with h-parameter ac equivalent circuit.
 - (b) Draw the circuit diagram of a transformer coupled class-A power amplifier. Obtain the expression for Maximum Conversion Efficiency ($\% \eta$). 2+3=5

- (c) Draw the circuit diagram of a feed back amplifier. Derive an expression for voltage gain of a feedback amplifier.
- (d) With the proper circuit diagram of a Hartley Oscillator explain its working principle. Write down the expression for generated frequency of the oscillator. Give one application of it.

4. Answer *any one* of the following questions:

6×1=6

- (a) Draw the circuit diagram of a single tuned voltage amplifier. Then obtain its h-parameters ac equivalent circuit. Hence derive the expression for voltage gain for this type of amplifier.

2+2+2=6

- (b) With proper circuit diagram obtain an expression for frequency of the generated signal for an R-C phase shift oscillator. What type of frequencies are generated by this oscillator?

2+3+1=6

- (c) Draw the circuit diagram of a Zener diode based voltage regulator for dc and explain its operation. How a constant dc voltage is obtained at its output?

2+2+2=6
