

B.Sc. 3rd Semester (Honours) Examination, 2019-20**ELECTRONICS****Course ID : 31712****Course Code : SHELC-302C-6(T)**

Course Title: Digital Electronics and Verilog (VHDL)

Time: 1 Hour 15 Minutes**Full Marks: 25**

*The figures in the right hand side margin indicate full marks.
Candidates are required to give their answers in their own words
as far as practicable.*

1. Answer *any three* of the following questions: 1×3=3
 - (a) Using 2's complement method subtract 1010_2 from 1101_2 .
 - (b) Convert the given hexadecimal number $(23A)_{16}$ to binary number.
 - (c) Find the decimal equivalent of the binary number 1010111 and 001011.
 - (d) Represent -14 in 1's complement form.
 - (e) What is a demultiplexer?

2. Answer *any three* of the following questions: 2×3=6
 - (a) Draw the symbol of an X-NOR gate and give its truth table.
 - (b) A Boolean expression is given as $Y = (A + B)(\bar{A} + \bar{B})$. Prove that this logic diagram is equivalent to an EX-OR gate.
 - (c) Prove the Boolean identity $AB + \bar{A}\bar{B} = \overline{\bar{A}\bar{B}} + \overline{AB}$.
 - (d) What is a decode counter?
 - (e) What are ripple counters?
 - (f) Write down the excitation table of S-R and J-K flip-flops.

3. Answer *any two* of the following questions: 5×2=10
 - (a) What is a Multiplexor? Explain the function of 8:1 MUX and design the same using different logic gates.
 - (b) What is a half-adder? Why is it so called? Design a half-adder by using Universal logic gates.
 - (c) Simplify the following Boolean function using Karnaugh mapping and draw the logical diagram using NAND gates only. $F(A, B, C, D) = \sum_m(0,1,2,4,7,8,9,12,13)$
 - (d) Write down the truth-table of half-subtractor. Design the same using NAND gates only.

4. Answer *any one* question:

6×1=6

- (a) Describe the operation of a 4 bit ripple counter using 4JK flip-flops. Draw the proper input output waveforms of the counter.
- (b) What is the need of clocking a flip-flop? Give the truth-table of a clocked SR flip-flop constructed with NAND gates and explain the operation of it.
- (c) Draw the basic circuit diagram of TTL NAND gate and explain its operation.
