

**BANKURA UNIVERSITY**

**B.Sc. 3<sup>rd</sup> Semester (Honours) Examination, March 2021**

**Subject: *Electronics (H)***

**Course ID: 31714**

**Course Code: SH/ELC/304/GE-3(TH)**

**Course Title: *Electronic Circuits and PCB Designing***

**Full Marks: 25**

**Time: 1 Hr 15 Min**

*(The figures in the right hand side margin indicate marks.*

*Answer all the questions)*

1. Answer *any three* of the following questions 1×3=3
  - a) State and explain KVL.
  - b) Draw a HWR circuit.
  - c) What is plated through holes technology?
  - d) What is the quiescent point of a transistor?
  - e) What do you mean by SMT?
  - f) What is a single sided board?
  
2. Answer *any three* of the following questions. 2×3=6
  - a) Describe the general rules of PCB Layout.
  - b) What do you mean by regulated power supply? Explain.
  - c) Explain CE characteristics of a transistor.
  - d) What do you mean by thermal runaway. Explain.
  - e) What is leakage current of a transistor. Define it. 1+1=2
  - f) What is etching process of a PCB?
  
3. Answer *any two* of the following questions. 5×2=10
  - a) What do you mean by basic artwork approach of a PCB? Explain.
  - b) State and explain photo resist and wet resist in the context of PCB designing. 2.5+2.5=5

c) What is etchant system? State the principles of solder connection.  
What are solder alloys? 2+2+1=5

d) Find the expression of efficiency of a FWR.

4. Answer *any one* of the following questions. 6×1=6

a) State and explain different stages of PCB designing.

b) Describe voltage divider biasing of a transistor with proper circuit diagram and their working.

c) Describe the SMT clearly depicting its benefits and limitations.