

**B.Sc. 3rd Semester (Honours) Examination, 2019-20****PHYSICS****Course ID : 32413****Course Code : SH/PHS/303/C-7**

Course Title: Digital System and Applications

**Time: 1 Hour 15 Minutes****Full Marks: 25**

*The figures in the margin indicate full marks.  
Candidates are required to give their answers in  
their own words as far as practicable.*

**Section-I**Answer *any five* of the following:

1×5=5

1. (a) Convert the hexadecimal number C5E2 into a binary number.
- (b) Prove that  $\overline{AB} + \overline{A} + AB = 1$ .
- (c) Explain the term 'SISO' for a shift register.
- (d) "A negative logic OR gate is equivalent to a positive logic AND gate"— Justify.
- (e) A device is needed to monitor the simultaneous occurrence of low states in two separate lines and to produce a high output as an indication. What will be the device?
- (f) Define linear ICs with example.
- (g) Write two applications of 555 timer.
- (h) Subtract  $(12)_{10} - (21)_{10}$  using 2's complement method.

**Section-II**Answer *any two* questions:

5×2=10

2. (a) What do you mean by digital comparator?  
(b) With truth table and proper explanation draw the circuit diagram of a single bit comparator. 1+4=5
3. Draw the circuit diagram of MSJK flip-flop using NAND gate only. Explain how can 'race around condition' can be solved using MSJK flip-flop. What is D-flip-flop? 1+3+1=5
4. What is a Synchronous counter? What is its advantage over asynchronous counter? Draw the block diagram of a 3-bit synchronous counter and explain its operation. 1+1+3=5
5. Distinguish between OR and EX-OR gate. Why EX-OR gate is called a coincidence checker? How X-OR gate is converted into EX-NOR gate? 2+2+1=5

**Section-III**

Answer *any one* question:

10×1=10

6. (a) Draw a 8 word × 4 bit ROM array using decoder and diodes. Explain its operation.
- (b) With block diagram of full adder and EX-OR gates, draw a circuit of 4 bit adder subtractor. Explain its operation. (2+4)+4=10
7. (a) Draw a BCD to decimal decoder circuit and explain its operation.
- (b) Show that  $(A \oplus B) \oplus C = A \oplus (B \oplus C)$ .
- (c) Simplify the Boolean expression  $Y = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$  using Karnaugh Map. 4+3+3=10
-