

M.Sc. 3rd Semester Examination, 2021
PHYSICS
Course Title : Advanced Electronics-II
Course Code : 304MEA
Course ID : 32454

Time: 2 Hour

Full Marks: 40

*The figures in the right hand side margin indicate full marks.
Candidates are required to give their answers in their own words
as far as practicable*

1. Answer *any five* of the following: 2×5=10
- (a) What is Darlington pair?
 - (b) Describe Epitaxial growth in IC technology.
 - (c) What is the necessity of feedback in op-amp?
 - (d) Write a program to subtract two numbers in assembly language.
 - (e) What is the duty of an ENABLE in a multiplexer?
 - (f) What is propagation delay? Explain with proper diagram.
 - (g) What is Fan-In and Fan-Out of a digital gate?
 - (h) Define the following in the context of gate:
 - i. $V_{IH(min)}$,
 - ii. $V_{IL(max)}$.
2. Answer *any four* of the following: 5×4=20
- (a) What are the steps of monolithic IC technology? Describe Oxidation.
 - (b) Describe acquisition range and tracking range of a Phase Locked Loop (PLL).
 - (c) Discuss the operation of an op-amp based square wave generator with suitable diagram.
 - (d) What is a multiplexer? Discuss with proper diagram and truth table a quadrupole two-input multiplexer. 1+4=5
 - (e) What do you mean by analog comparators? Discuss its operation. 2+3=5
 - (f) Discuss the circuit operation of a Widler current source.

3. Answer *any one* of the following:

10×1=10

(a) (i) Derive the intrinsic gain of a common-source (CS) amplifier with current-source load.

(ii) Find the output resistance of a source-degenerate CS amplifier.

(iii) Obtain the gain of a current-mirror circuit.

3+3+4=10

(b) Describe the operation of an inverting precision full-wave rectifier with proper figures.

10
