

B.Sc. 4thSemester (Honours) Examination, 2021-22**PHYSICS****Course ID: 42413****Course Code: SHPHS/403/C-10/T-10****Course Title: Analog Systems and Applications (T-10)****Time: 1Hour 15 Minutes****Full Marks: 25***The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words**As far as practicable***Section-I**1. Answer any *five* questions:

1×5 = 5

- (a) Write down the relation between α and β of transistor.
- (b) What is CMRR?
- (c) What is the characteristic of class B amplifier?
- (d) What is virtual ground?
- (e) Mention two important advantages of using Si over Ge for semiconductor device.
- (f) Explain the static and dynamic resistance of a semiconductor diode.
- (g) State Barkhausen's criterion for self-sustained oscillation.
- (h) Give example of a device which shows negative resistance?

Section-II2. Answer any *two* questions:

5×2 = 10

- (a) Draw the circuit diagram of a RC phase shift oscillator and find its operating frequency. 2+3
- (b) Define ripple factor. Find the ripple factor of a bridge rectifier. 1+4
- (c) State the principle of operation of LED showing the band diagram. Write down the difference between LED and Photodiode. 4+1
- (d) Drawing a proper circuit diagram and explain how OP-AMP can be used as logarithmic amplifier. 2+3

Section-III3. Answer any *one* question:

10×1 = 10

- (a) i. Draw the I-V characteristic of JFET and explain it. What is pinch-off voltage? 2+2+1
- ii. Calculate the values of I_C and I_E for a transistor with $\alpha_{dc} = 0.99$ and $I_{CBO} = 5\mu A$. I_B is measured as $20\mu A$. 2+3
- (b) Draw the frequency response of RC coupled amplifier and explain the graph. Draw the h parameter equivalent circuit of two stage RC coupled amplifier and find its mid frequency gain. (2+3+2+3)