

BANKURA UNIVERSITY

B.Sc. 5th Semester (Honours) Examination, March 2021

Subject: *Electronics (H)*

Course ID: 51716

Course Code: SH/ELC/503/DSE-1(TH)

Course Title: *Power Electronics*

Full Marks: 25

Time: 1 Hr 15 Min

(The figures in the right hand side margin indicate marks.

Answer all the questions)

1. Answer *any three* of the following questions: 1×3=3
 - a) What do you mean by “rating” of an SCR?
 - b) Power BJT is a current controlled device. Why?
 - c) What is meant by forced commutation?
 - d) What is meant by duty-cycle?
 - e) What is the main drawback of a single phase half bridge inverter?
 - f) What are the two configuration of single phase 2 pulse controlled rectifier?

2. Answer *any three* of the following questions: 2×3=6
 - a) Explain the terms $\frac{dv}{dt}$ rating and $\frac{di}{dt}$ rating of an SCR.
 - b) Mention two drawbacks of GTO?
 - c) Why circuit turn off time should be greater than the thyristor turn-off time?
 - d) What is meant by inverter? What are the applications of an inverter? 1+1
 - e) Give the full form of the following: IGBT, PUT, RCT, SCS.
 - f) What is meant by inversion mode in single phase fully controlled converter?

3. Answer *any two* of the following questions: 5×2=10
- a) Explain different modes of operation of thyristor with the help of static V-I characteristics.
 - b) What is a power transistor? With a neat sketch, explain its basic structure. Draw its I-V characteristics. What is second breakdown? 1+2+1+1
 - c) With a neat circuit diagram, explain the principle of operation of a 1- ϕ half bridge inverter and derive an expression for the rms value of fundamental component of load voltage. 1+2+2
 - d) How do you protect the thyristors from over voltages and over currents? Explain the various protection schemes used. 2.5+2.5
4. Answer *any one* of the following questions: 6×1=6
- a) Explain the operation of step down chopper with a neat circuit diagram and necessary waveforms. Also derive expression for output voltage. 4+2
 - b) If a purely resistive load is supplied through single phase half wave controlled converter and $\alpha = \frac{\pi}{2}$, determine (i) Form factor, (ii) Rectification efficiency, and (iii) Ripple factor. 2+2+2
 - c) Explain the operation of single phase fully controlled bridge converter with R load. Obtain the expressions for average and rms value of output voltage with relevant waveform. 2+2+2