

BCA Semester-II (Hons) Examination, 2022-23**BACHELOR OF COMPUTER APPLICATION**

Course ID : 23311

Course Code : CC-03

Course Title : Digital Logic

Time : 2 Hours

Full Marks : 50

*The figures in the right-hand margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.***GROUP - A**

1. Choose the best alternative from the following options for each question: $1 \times 10 = 10$


- i) A Boolean function $x'+y'+xy+x'y$ is equivalent to-
- $x'+y'$
 - $x+y$
 - $x+y'$
 - $x'+y$
 - None of the above
- ii) In an SR latch made by cross coupling two NAND gates, if both S and R inputs are set to 0 then it will result in

- $Q=0, Q'=1$
- $Q=1, Q'=0$
- $Q=1, Q'=1$
- Indeterminate states
- None of the above

iii) The hexadecimal representation of 657_8 is:

- 1AF
- D78
- D71
- 32F
- None of the above.

 iv) Consider the following circuit, which one of the following is TRUE?



- f is independent of x
- f is independent of y
- f is independent of z
- the value of f is 1
- None of the above.

- v) What value is to be considered for don't care condition?
- 0
 - 1
 - Either 0 or 1
 - Any number except 0 and 1
 - None of the above
- vi) Suppose only one multiplexer and one inverter are allowed to be used to implement any Boolean function of n variables. What is the minimum size of the multiplexer needed?
- 2^n lines to 1 line
 - 2^{n+1} lines to 1 line
 - 2^{n-1} lines to 1 line
 - 2^{n-2} lines to 1 line
 - None of the above.
- vii) Race around condition is avoided in-
- JK Flip flop
 - Master Slave Flip flop
 - SR Flip flop
 - SR latch
 - None of the above.

- viii) The size of PLA is specified by number of-
- Inputs
 - Product terms
 - Outputs
 - All of the above
 - None of the above.
- ix) Consider the following function:
- $$F_1 = \Sigma(1,2,4,8,10,14)$$
- $$F_2 = \Sigma(2,5,9,11)$$
- $$F_3 = \Sigma(2,4,5,6,7)$$
- The minimum configuration of the decoder should be
- 2×4
 - 3×8
 - 4×16
 - 5×32
 - None of the above.
- x) The operation which is commutative but not associative is:
- AND
 - OR
 - EX-OR
 - NAND
 - None of the above.

GROUP-B


2. Answer any **five** questions: $2 \times 5 = 10$
- Explain Minterm and Maxterm.
 - Differentiate positive and negative logic system.
 - Express any one the following decimal numbers in 2421 and 5421 codes:
 - 6734
 - 3421
 - What is non Weighted code? How it differ from weighted code?
 - What is the function of a multiplexer's select inputs?
 - What is shift register? Name the different types of shift registers.
 - What is meant by edge triggering?
 - Explain the difference between the performance of asynchronous and synchronous counters.

GROUP-C

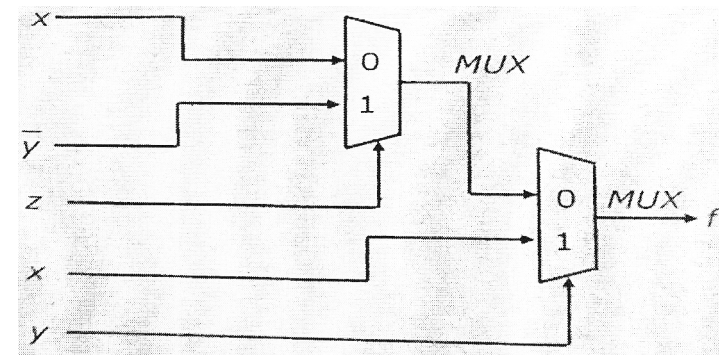3. Answer any **four** questions: $5 \times 4 = 20$
- A circuit outputs a digit in the form of 4 bits. 0 represented by 0000, 1 by 0001 ... 9 by 1001. A combinational circuit is to be designed which takes these 4 bits as inputs and outputs 1 if the

digit ≥ 5 , and 0 otherwise. If only basic gates are used then what is the minimum number of gates required. Draw the circuit diagram and truth table.

- Prove that:
 - $BCD + A'C'D' + ABD = BCD + A'C'D' + ABC'$
 - $A'B'C' + A'B'C + A'BC' + A'BC + AB'C' = A' + (B+C)'$
- Consider the following circuit below. Write down the output of the circuit :



- Design a full adder circuit using two half adder. Write down the truth table of full adder.
- Explain how a J-K flip flop can be converted into a D flipflop.
- Draw the logic diagram of three bit synchronous binary up-counter.

GROUP-D

4. Answer any **one** from the followings: $10 \times 1 = 10$

- i) a) Simplify the Boolean function using Quine McClusky method :

$$F(W, X, Y, Z) = \Sigma_m(1, 3, 4, 5, 9, 10, 11) + \Sigma_d(6, 8)$$

- b) Implement the function using decoder:

$$F(A, B, C) = \Sigma_m(1, 3, 5, 6) \quad 6+4$$

- ii) a) Write truth table, circuit diagram and excitation table of T-flip flop.

- b) Write a short note on parallel-in-parallel-out shift register. $6+4$
