

B.Sc. Semester-IV Examination, 2022-23
ELECTRONICS [Honours]

Course ID : 41711 Course Code : SH/ELC/401/C-8(T-8)


Course Title : Operational Amplifiers and Applications

Time : 1 Hour 15 Minutes Full Marks : 25


The figures in the right-hand margin indicate marks.

Candidates are required to give their answers in their own words as far as practicable.

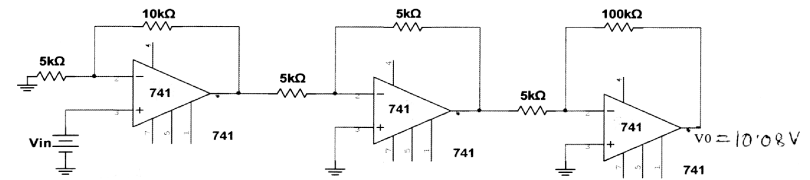
1. Answer any **three** of the following: 1×3=3
 - a) Draw the voltage transfer curve of an ideal and practical op-amp.
 - b) What is Zero Crossing Detector (ZCD)?
 - c) Why is op-amp called operational amplifier?
 - d) What is differential amplifier?
 - e) Draw the circuit diagram of sample and hold circuit.
 - f) The gain of buffer amplifier is unity.– Explain.
2. Answer any **three** of the following: 2×3=6
 - a) Calculate the input voltage if the final output V_0 is 10.08 volts.



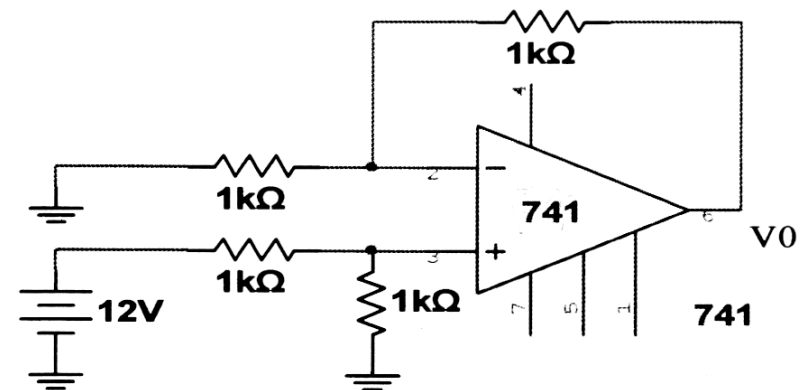- b) With a neat circuit diagram, show how can you obtain an output which is proportional to the multiplication of two input signals.
- c) What is op-amp Integrator? Sketch the output of an op-amp integrator if the input is a step signal.
- d) Define the following terms: Slew Rate (SR), SVRR.
- e) What are differential gain and common mode gain of a differential amplifier?
- f) Find the output voltage of the following circuit:



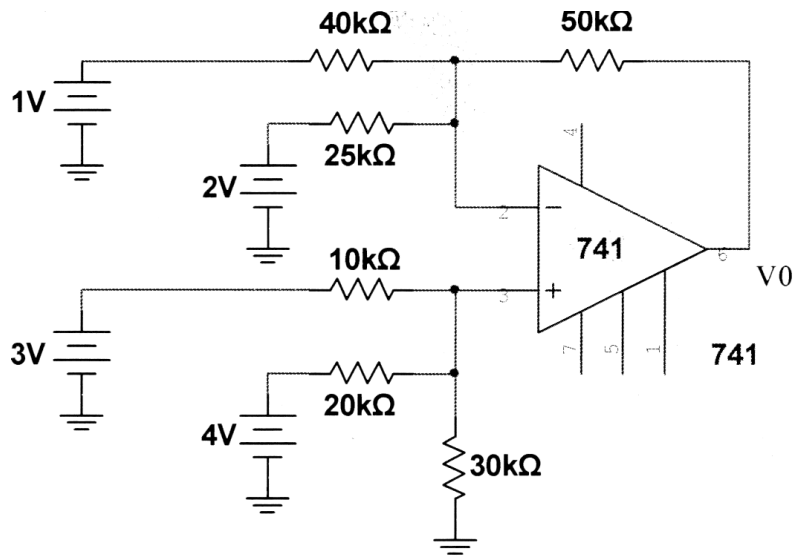3. Answer any **two** of the following: $5 \times 2 = 10$
- Draw the functional diagram of IC 555 Timer. Explain with a circuit diagram how it can be connected for monostable operation.
 - Draw the circuit diagram of an inverting Schmitt trigger and explain its operation with the help of hysteresis curve.
 - A differential amplifier has inputs $V_1 = 10 \text{ mV}$ and $V_2 = 9 \text{ mV}$. It has a differential mode gain of 60 dB and a CMRR of 80 dB. Find the percentage error in the output voltage and the error voltage.
 - Find V_0 of the following circuit:



4. Answer any **one** of the following: $6 \times 1 = 6$
- Draw the circuit of a symmetrical emitter-coupled differential amplifier and derive expression for CMRR. 6
 - Explain the first order low-pass Butterworth filter with a neat circuit. Derive its frequency response. Also design the same filter with higher cut-off frequency of 2 KHz and pass band gain of 5. $4+2=6$
 - With the neat circuit diagram, explain the working of Wien bridge oscillator using op-amp. Hence, derive the expression of oscillation frequency and gain of the amplifier. $2+4=6$