

**B.Sc. Semester-IV Examination, 2022-23****PHYSICS [Honours]**

Course ID : 42413 Course Code : SH/PHS/403/C-10(T10)

Course Title : Analog Systems and Applications

Time : 1 Hour 15 Minutes

Full Marks : 25

*The figures in the right-hand margin indicate marks.**Candidates are required to give their answers in their own words as far as practicable.***SECTION-I**

1. Answer any **five** questions: 1×5=5
- Why do Si or Ge diodes not emit light but GaAs diode does?
  - In an n-p-n transistor, 95% of emitted electrons reach to collector. If the collector current is  $19\mu A$ , then determine the value of base current.
  - Draw the output characteristics curves of an n-p-n transistor in CE mode. Indicate the active, cut-off and saturation regions on the output curves.
  - A p-n junction Ge diode has the reverse saturation current of  $1.5\mu A$  at 300 K. Obtain the dynamic resistance of the diode at that temperature for an applied forward voltage of 0.3 V.

*[Turn Over]*


- Why a transistor cannot be made by joining two diodes back to back?
- An n-channel JFET has  $I_{DSS} = 12$  mA. If the pinch off voltage  $V_p = -4V$ , find the drain current for  $V_{GS} = -2V$ .
- Why filters are used at the output of a rectifier system?
- What is fundamental principle inherent for the action of a Photodiode?

**SECTION-II**

2. Answer any **two** questions: 5×2=10
- Draw a neat circuit diagram for a full wave rectifier and explain its operation. Calculate the efficiency of rectification of the full wave rectifier. 1+2+2
  - Discuss the operation and working of a Zener diode and a real example of its use. Draw the energy level diagram for unbiased p-n junction. (1+2+1)+1
  - What is early effect? What is punch through in a transistor?
    - Find the transistor currents and  $V_{CE}$  in the following circuit with silicon transistor of  $\beta$  value 100 and negligible  $I_{co}$ . 1+1+3

463/Phs.

( 2 )

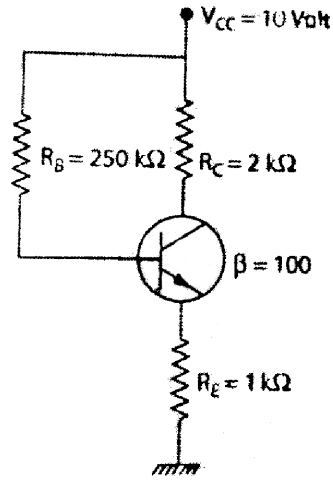

- d) What do you mean by feedback in amplifier? What do you mean by positive and negative feedback? Find the relation between the open loop gain and closed loop gain of a negative feedback amplifier.

1+(1+1)+2

### SECTION-III

3. Answer any **one** question: 10×1=10
- a) i) Draw the h-parameter equivalent circuit of two stage RC coupled amplifier and find its mid frequency gain.
- ii) The mid frequency gain of a RC coupled amplifier is 120. At frequency 100 Hz and 100 kHz, the gain falls to 60. Determine the lower and upper cut-off frequencies.

- iii) Define frequency distortion in an amplifier.
- iv) The output voltage of an amplifier is 10 V at 5 kHz and 70.07 V at 25 kHz. What is the decibel change in the output power level?

5+3+1+1

- b) Why OP-AMP is so called? What is common mode rejection ratio of an OP-AMP? How do the characteristics of a practical OP-AMP differ from that of an ideal OP-AMP? Explain how an OP-AMP may be used as (i) differentiator (ii) integrator.

1+1+2+3+3